

IMPORTANT NOTICE




If your Motorola Amplified Speaker bracket and PC board do *not* look like the examples shown below, there is a significant chance that the PC board described in the following pages will NOT fit into the speaker case properly. In that case, contact me, NØSS, for a possible alternate PC board design which might fit. I do have a design for a slightly newer version of the same amplified speaker.

Speaker ID Nomenclature Information:




Etched into Foil side of board: 84E83475N01

Stamped (in black) on solder side of board: TRN5276A

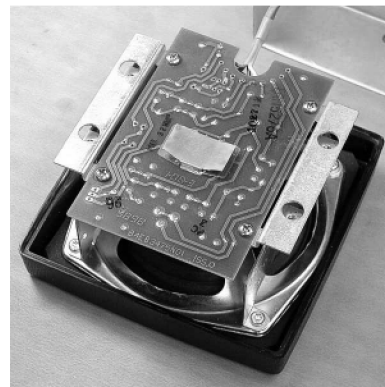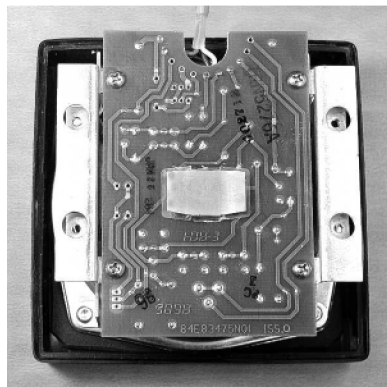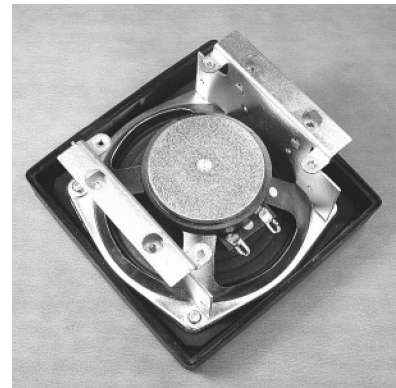Stamped (in black) on back of speaker case: TLN2435A



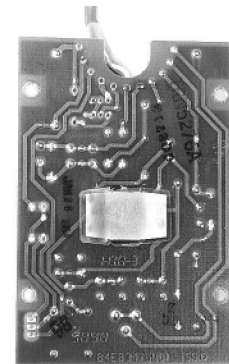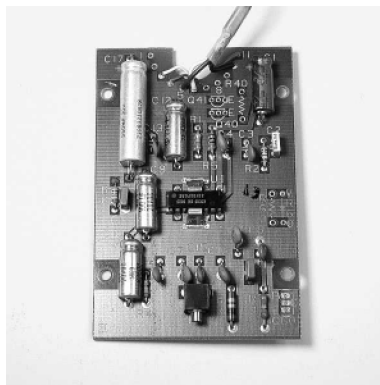
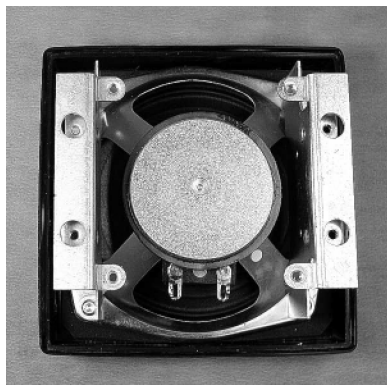
Note the design of the PC board support frame. The PC board fits INSIDE the frame, supported by the two inner tabs.




TDA2003 5W AF Amp

This PC board was specifically designed to fit into an 'older-style' Motorola Amplified Speaker Enclosure. See previous page for further reference info.


by: Tom Hammond, NØSS, 02/10/2004

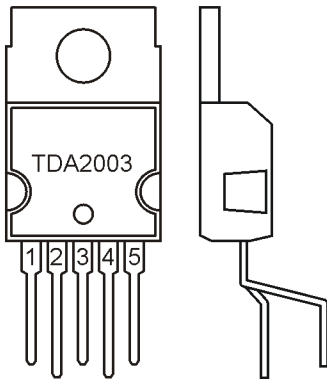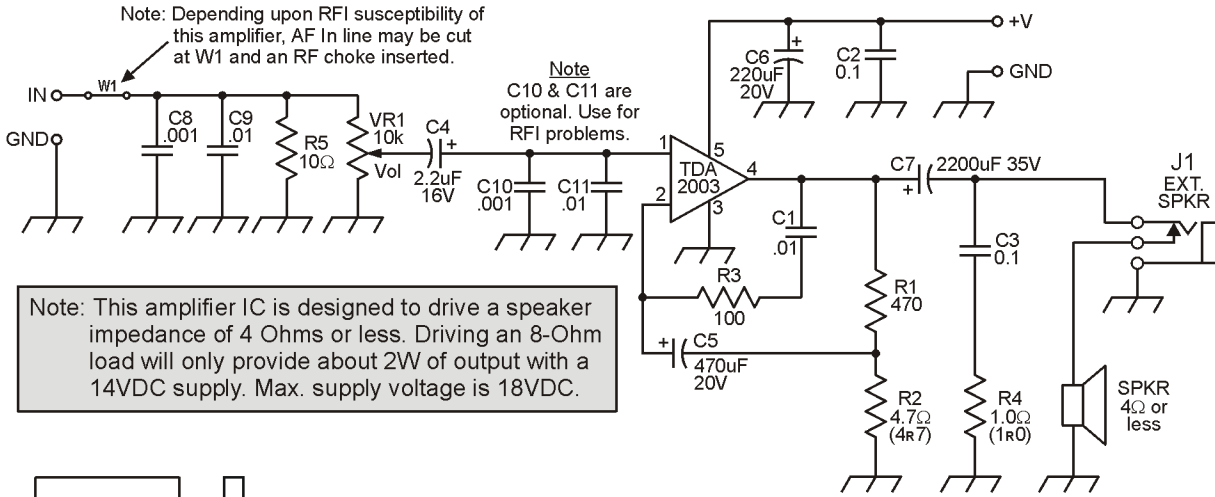

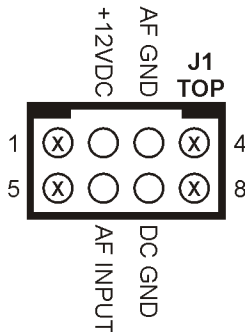- 5 - Vss
- 4 - Output
- 3 - Gnd
- 2 - Inverting Input
- 1 - Non-Inverting Input



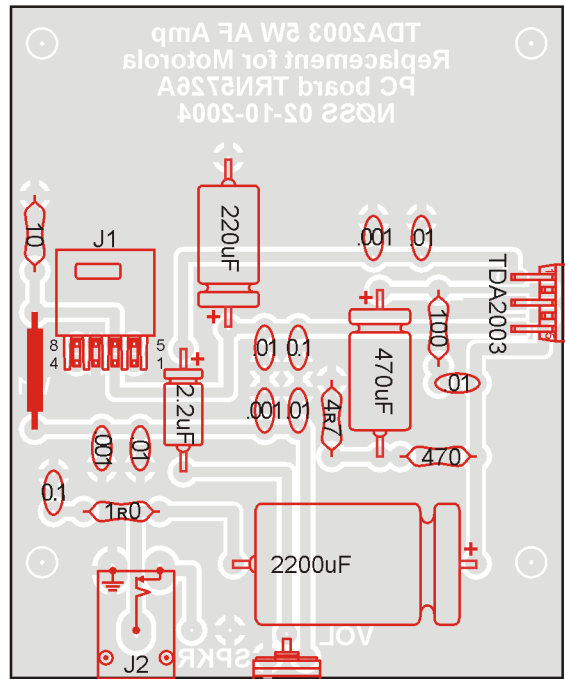Note: Because the decimal point is so difficult to see on the parts placement diagram, the 1.0Ω and the 4.7Ω resistors are labeled "1r0" and "4r7".



PC board as viewed from component side


Attach the (grounded) TAB of the TDA2003V to the PC board mounting frame.

PC Board cut size: 3-1/2" H x 2-7/8" W

VERY IMPORTANT ASSEMBLY NOTE

Install the TDA2003 IC LAST. When installing the TDA2003V IC, insert it into the holes in the PC board, but **DO NOT SOLDER**. Then install the PC board onto the frame of the speaker and attach the tab of the TDA2003V to the frame (which will be used as the heatsink). Once both the PC board *and* the IC are installed, solder the IC to the PC board.

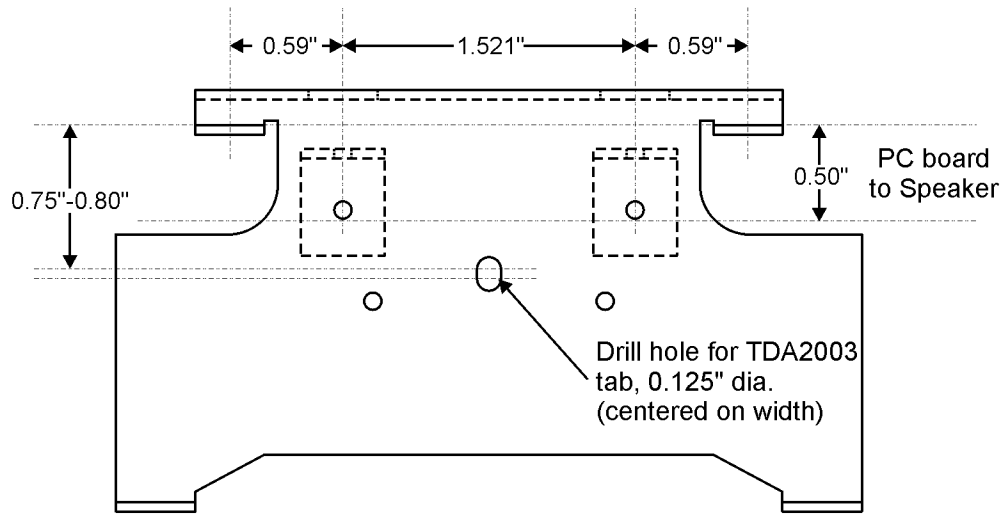This is a scale drawing of the PC board support brackets in the Motorola Amplified Speaker. It was used to design this PC board wherein the bracket is used as the heat-sink for the TDA2003 AF Amplifier IC.




Factory Specification Performance Data

source: <http://www.st.com/stonline/books/pdf/docs/1449.pdf>


TDA2003

Output power vs. supply voltage

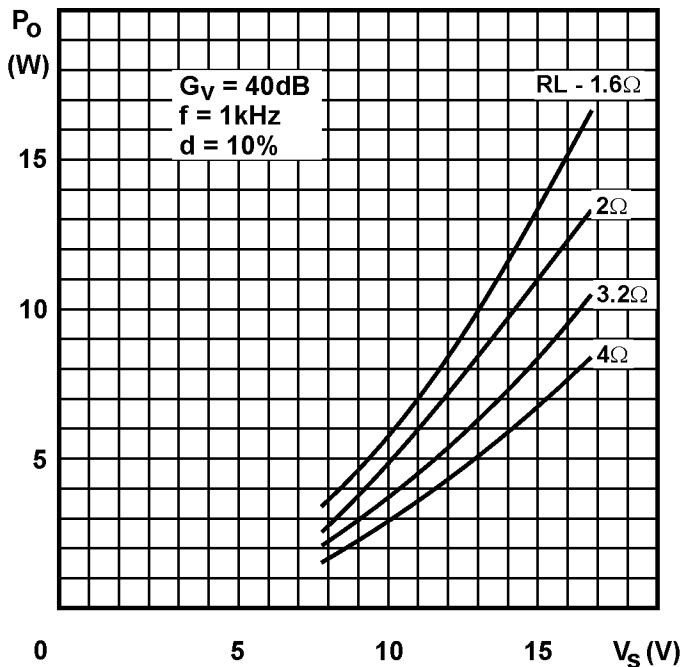


TDA2003

Output power vs. load resistance

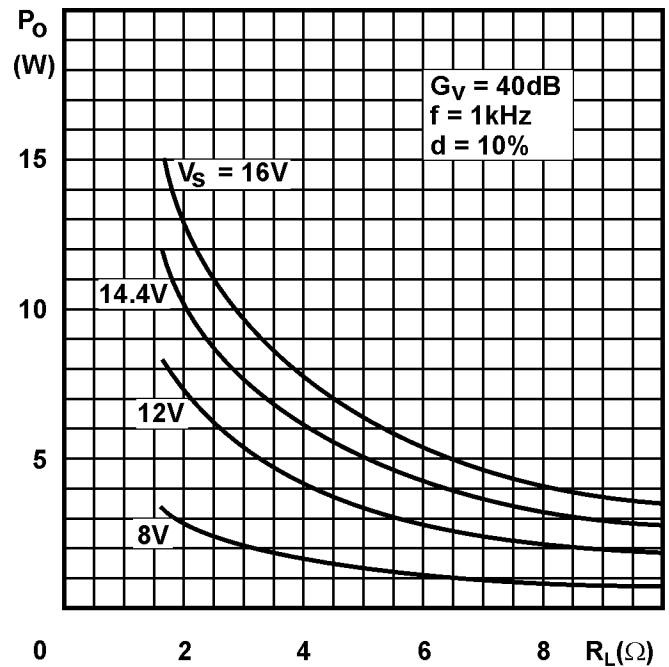

TDA2003

Power dissipation and efficiency vs. output power ($R_L = 4\Omega$)

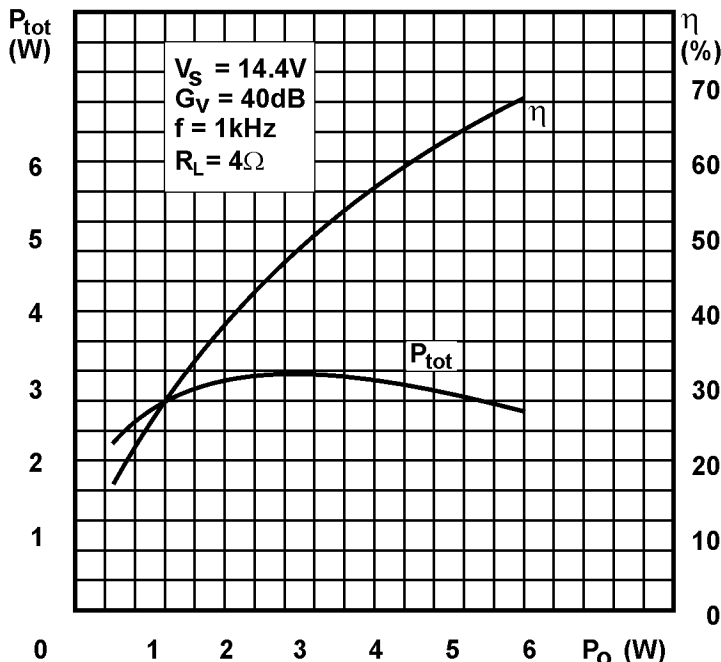

TDA2003

Power dissipation and efficiency vs. output power ($R_L = 2\Omega$)

